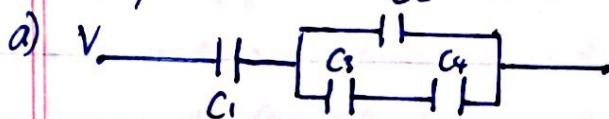


1. Simplify the circuit



$$C_1 = 3F, C_2 = 4F \\ C_3 = 6F, C_4 = 3F \quad V = 10V$$

See $C_5 = [C_3, C_4]$ system, thus $C_5 = \left(\frac{1}{C_3} + \frac{1}{C_4}\right)^{-1} = 2F$

$C_6 = [C_2, C_5]$ system, thus $C_6 = C_2 + C_5 = 6F$

$G_{\text{parallel}} = [C_1, C_6]$ system, $G_{\text{parallel}} = \left(\frac{1}{C_1} + \frac{1}{C_6}\right)^{-1} = 2F$

$$Q_{\text{parallel}} = G_{\text{parallel}} \cdot V = 10V \cdot 2F$$

$$V_1 = \frac{Q}{C_1} = \frac{20}{3}V.$$


$$V_2 = V - V_1 = 10 - \frac{20}{3} = \frac{10}{3}V.$$

$$V_3 + V_4 = V_2 = \frac{10}{3}V \Rightarrow Q_3 = Q_4 = C_3 \cdot V_3 = C_4 \cdot V_4 = \frac{V_3}{V_4} = \frac{C_4}{C_3} = \frac{3}{6} = \frac{1}{2}.$$

$$\text{Thus } V_3 = \frac{10}{3} \times \frac{1}{1+2} = \frac{10}{9}V \quad V_4 = \frac{10}{3} \times \frac{2}{3} = \frac{20}{9}V$$

There is no current through the capacitors. $I_{C_i} \quad [i \in \{1, 4\}] = 0$

b) Simplify the circuit

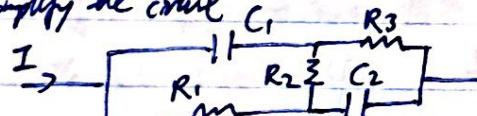

$$C_1 = 6F, C_2 = 6F \quad R_2 = 3\Omega \\ R_1 = 1.5\Omega, R_3 = 1.5\Omega \quad I = 6A$$

There is no current through capacitors. $I_{C_1} = I_{C_2} = 0$

The resistors are in series. Thus $R_{\text{parallel}} = R_T = R_1 + R_2 + R_3 = 6\Omega \quad V_{\text{parallel}} = I \cdot R_{\text{parallel}} = 6V$

$$\text{Thus } V_{R_1} = \frac{R_1}{R_T} \cdot V_T = \frac{1}{4} \cdot 24V = 6V. \quad I_{R_1} = I = 6A$$

$$V_{R_2} = \frac{R_2}{R_T} V_T = \frac{1}{2} \cdot 24V = 12V \quad I_{R_2} = I = 6A. \quad / \quad V_{R_3} = \frac{R_3}{R_T} V_T = \frac{1}{4} \cdot 24V = 6V. \quad I_{R_3} = I = 6A$$

$$V_{C_1} = \frac{R_1 + R_2}{R_T} \cdot V_T = V_{R_1} + V_{R_2} = 18V.$$

$$V_{C_2} = V_{R_2} + V_{R_3} = 18V$$

2. Basic Amplifier Building Blocks.

- a) Denote the node between R_1 and R_2 as node A.

Since the left side of R_1 is connected to ground.

we have voltage at node A = $\frac{R_1}{R_1+R_2} \cdot V_o$

Since the two inputs of the amplifier are equal. $V(\text{Node A}) = V_s$.

thus $V_s = V_s \cdot \frac{R_1+R_2}{R_1}$

Thus the gain of the amplifier is $\frac{V_o}{V_s} = \frac{R_1+R_2}{R_1} > 0$.

Name: non-inverting amplifier.

Origin: Gain of the amplifier is positive, which means that it doesn't invert the signal of input.

- b) Denote the node on the right side of R_1 as A.

Since the inputs of the amplifier are equal (in voltage). $V(\text{Node A}) = 0$.

Thus, since current through R_1 = current through R_2 .

$$\frac{V_s - 0}{R_1} = \frac{0 - V_o}{R_2} \Rightarrow V_o = -\frac{R_2}{R_1} V_s$$

The gain of the amplifier is $\frac{V_o}{V_s} = -\frac{R_2}{R_1} < 0$

Name: inverting amplifier.

Origin: Voltage gain of the amplifier is negative, which means that it inverts the signal of input.

3. Amplifier with Multiple Inputs.

a) Denote the node on the right side of R_1 as A.

Since the voltage at the two inputs of the amplifier must be equal.

$$V_- = V_+ = 0 \text{ v} \quad (\text{since } V_+ \text{ is connected to GND}) \text{, thus } V_A = 0$$

Thus, no current nor voltage flows through R_1 .

Denote the node on the left side of R_2 as B.

$$\text{since, the right side of } R_2 \text{ is } 0 \text{ v}, \quad V_B = V_{O1}$$

Thus, the line -GND- R_3 - R_2 - \Rightarrow is is current through R_3 and R_2 .

$$\text{thus, } i_s = \frac{V_B - 0}{R_2} = \frac{V_{O1}}{R_2}$$

$$\text{thus, } V_{O1} = i_s \cdot R_2$$

b) Golden Rule: $V_- = V_+ = V_{S2}$

Denote the node on the right of R_1 as A. then $V_A = V_{S2}$

since R_1 is in series and the left of R_1 is GND.

Denote the left of R_2 as node B. then $V_B = V_{O2}$.

$$\text{thus, } \frac{R_1}{R_1 + R_2} \cdot V_{O2} = V_{S2} \Rightarrow V_{O2} = V_{S2} \cdot \frac{R_1 + R_2}{R_1} = V_{S2}(1 + \frac{R_2}{R_1})$$

c) Golden Rule: $V_- = V_+ = V_{S2}$. Denote the right of R_1 as node A. then $V_A = V_{S2}$

$$\text{By KCL: } \frac{V_A - V_{S1}}{R_1} + i_s + \frac{V_A - V}{R_2} = 0 \quad (\text{Denote the left of } R_2 \text{ as node B, then } V_B = V_0)$$

$$\text{thus, } \frac{V_{S2} - V_{S1}}{R_1} + i_s + \frac{V_{S2} - V_0}{R_2} = 0 \Rightarrow \frac{V_0 - V_{S2}}{R_2} = -\frac{V_{S1} + V_{S2}}{R_1} + i_s$$

$$\Rightarrow V_0 = \frac{R_2}{R_1} (V_{S2} - V_{S1}) + R_2 \cdot i_s + V_{S2}$$

$$= \frac{R_1 + R_2}{V_{S2}} + R_2 \cdot i_s - \frac{R_2}{R_1} \cdot V_{S1}$$

d) No. V_B doesn't change between port (a) and the port. [if V_B still mean]
 No change $V_{B,\text{new}}$ doesn't depend on R_2 .

If V_B still mean the voltage at the output (depends on the right side of R_2) then V_B do not change; if we compare V_B and $V_{B,\text{new}}$ then they are different.

Denote the node at the right side of R_2 as A.

$$\text{Thus, } V_A = \frac{R_1+R_2}{R_2} \cdot V_{S2} + R_2 \cdot i_S - \frac{R_2}{R_1} \cdot V_{S1}$$


Since $V_- = V_+$ for the second op-amp. Hence the node on the top of R_2 as B.
 thus $V_B = V_A$

Hence the node on top of $R_3 = C$, thus $V_C = V_{B,\text{new}}$.

$$\text{Thus, (since no current enter op-amp). } \frac{R_4}{R_3+R_4} \cdot V_{B,\text{new}} = V_B = V_A$$

$$\text{Thus } V_{B,\text{new}} = \frac{R_3+R_4}{R_4} \left(\frac{R_1+R_2}{R_2} \cdot V_{S2} + R_2 \cdot i_S - \frac{R_2}{R_1} \cdot V_{S1} \right)$$

4. Op-Amp Golden Rules.

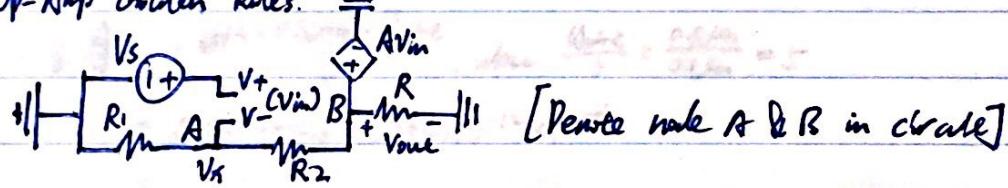

$$\text{Thus } V_A = V_Ain, \quad V_B = AV_{Ain} = V_{out} = A(V_+ - V_-) = (V_S - V_T)A$$

Since $R_{in} = \infty$, no current between V_+ and V_-

$$\text{Thus, } V_A = \frac{R_1}{R_1+R_2} \cdot V_B = \frac{R_1}{R_1+R_2} \cdot A(V_S - V_T)$$

$$\text{Then, } \frac{V_S - V_T}{V_A} = \frac{R_1+R_2}{A R_1} = \frac{V_S}{V_A} - 1 \Rightarrow \frac{V_S}{V_A} = \frac{A R_1 + R_1 + R_2}{A R_1} \Rightarrow V_A = \frac{A R_1 \cdot V_S}{A R_1 + R_1 + R_2}$$

Since $\frac{V_A}{V_S} = \frac{A R_1}{A R_1 + R_1 + R_2} < 1$. V_A is smaller than V_S .

$$\text{And } V_{out} = A(V_S - V_A) = A V_S \left(\frac{R_1+R_2}{A R_1 + R_1 + R_2} \right)$$

The output doesn't depend on R .

b) When $A \rightarrow \infty$, $V_T = \frac{AR_1 \cdot V_S}{AR_1 + R_2} = V_S \frac{1}{1 + \frac{R_2}{AR_1}} \Rightarrow \text{since } \frac{R_2}{AR_1} \rightarrow 0, \Rightarrow V_T \rightarrow V_S$

 $V_{out} = AV_S \left(\frac{R_1 + R_2}{AR_1 + R_2} \right) = \frac{AV_S}{\frac{AR_1}{R_1 + R_2} + 1} = V_S \frac{1}{\frac{R_1}{R_1 + R_2} + \frac{1}{A}} \Rightarrow \text{since } \frac{1}{A} \rightarrow 0, V_{out} \rightarrow V_S \frac{1}{\frac{R_1}{R_1 + R_2}} \rightarrow V_S \frac{R_1 + R_2}{R_1}$

By Gohden Rule

 $V_+ = V_S = V_- = V_T, \text{ [same]}$

Since no current between V_T and V_- . By KCL: $\frac{V_T - 0}{R_1} + \frac{V_T - V_{out}}{R_2} = 0$

Thus $V_T R_2 + V_T R_1 = V_{out} R_1 \Rightarrow V_{out} = \frac{R_1 + R_2}{R_1} V_T, \text{ [same]}$

These answers are the same.

5. Dynamic Random Access Memory (DRAM)

a) $Q_{initial} = Q_{bit} = C_{bit} \cdot V_{bit} = 18 \times 10^{-15} \times 1.2 = 2.16 \times 10^{-14} C$

In order to hold $V > 2.9$ after 1ms. we must have $I_{leak} \cdot 1ms \leq 0.4V \cdot C_{bit}$

Thus, in maximum, $I_{leak} = \frac{2.16 \times 10^{-14}}{3} / 1 \times 10^{-3} = 7.2 \times 10^{-12} A$

b) $C = \varepsilon \frac{A}{d} = \varepsilon \frac{1024 \times 0.5 \mu m \cdot \lambda_{bit}}{S}, \text{ where } \frac{\lambda_{bit}}{S} = \frac{0.5 \mu m}{0.1 \mu m} = 5$
 $= 5 \times 1024 \times 0.5 \times 8.854 \times 10^{-12} \times 10^{-6}$
 $= 2.267 \times 10^{-14}$

c) ① On. [$V_{bit} = 0V$ initially]

② since $Q = C_{bit} V_{bit}$, after S_1 is switched $V_{bit} = V_{bitm} = V_{cell}$ [$V_{bit} = 1.2V$ initially]

thus: $V_{bitm} C_{bit} + V_{bitm} C_{bitm} = C_{bit} V_{bit}$

$$V_{bitm} = \frac{C_{bit} V_{bit}}{C_{bit} + C_{bitm}} = \frac{18 \times 10^{-15} \times 1.2}{(1800 + 2.3125) \times 10^{-15}} = 0.56842 V$$

d) $C_{bitm} = \varepsilon \frac{A}{d} = 5 \times 0.5 \times 9.8146 \times 10^{-12} \times 10^{-6} \times n \cong 2.3125 \times 10^{-17} n$

$$V_{bitm} = \frac{C_{bit} \cdot V_{bit}}{C_{bit} + C_{bitm}} = \frac{1800 \times 1.2}{1800 + 2.3125 n} \geq 0.4 \Rightarrow 2160 \geq 720 + 0.927 n$$

$$\Rightarrow n \leq 153.4 \quad \text{Ans (cell number) max} = 153$$

b. It's finally raining

a) Since $C = \frac{\Sigma A}{\Delta t}$

when it's empty: $C_{empty} = \frac{\epsilon (w \cdot h_{tot})}{w} = \epsilon \cdot h_{tot}$

when it's full: $C_{full} = \frac{81\epsilon \cdot (w \cdot h_{tot})}{w} = 81\epsilon \cdot h_{tot}$

b) $G_{tot} = (C_{tot} + C_{air} = \frac{81\epsilon \cdot w \cdot h_{tot}}{w} + \frac{\epsilon \cdot w \cdot (h_{tot} - h_{air})}{w} = 81\epsilon h_{tot} + \epsilon (h_{tot} - h_{air}) = \epsilon (h_{tot} + 80h_{air})$



$$C_{tot} = C_T = \left(\frac{1}{C_{air}} + \frac{1}{C_{water}} \right)^{-1} = \frac{C_{air} \cdot C_{water}}{C_{air} + C_{water}}$$

Since in series, $Q_{tot} = Q_{water} = Q_{air} = V_{in} \cdot C_T = \frac{C_{air} \cdot C_{water}}{C_{air} + C_{water}} \cdot V_{in}$.

Phase 2:

$$Q_T = Q_{tot} + Q_{water} = 2 \times Q_{air} = V_{out} (C_{tot}^2) = V_{out} (C_{air} + C_{water}) = 2V_{in} \frac{C_{air} \cdot C_{water}}{C_{air} + C_{water}}$$

thus $V_{out} = 2V_{in} \frac{C_{air} \cdot C_{water}}{(C_{air} + C_{water})^2}$

d) Done

e) $\frac{2V_{in}}{V_{out}} = \frac{(C_{air} + C_{water})^2}{C_{air} \cdot C_{water}} = (C_{air} + C_{water}) \left(\frac{1}{C_{air}} + \frac{1}{C_{water}} \right) = 2 + \frac{C_{water}}{C_{air}} + \frac{C_{air}}{C_{water}}$

$$C_{water} = C_{empty} = \epsilon \cdot h_{tot}, \text{ thus } \frac{C_{air}}{C_{empty}} = \frac{h_{tot} + 80h_{air}}{h_{tot}}$$

$$\text{thus } \frac{C_{air}}{C_{empty}} = \eta, \quad \eta + \frac{1}{\eta} + 2 = \frac{2V_{in}}{V_{out}} \Rightarrow \eta + \frac{1}{\eta} = \frac{2V_{in}}{V_{out}} - 2 = k \text{ (define as)}$$

$$\eta + \frac{1}{\eta} = b, \quad \Rightarrow \eta^2 - b\eta + 1 = 0 \Rightarrow \eta = \frac{b \pm \sqrt{b^2 - 4}}{2} \quad \text{since } C_{air} \geq C_{empty} \text{ since } C_{air} = 1 + \epsilon \cdot 80 \cdot h_{tot}$$

$$\text{thus } \eta = \frac{b + \sqrt{b^2 - 4}}{2}, \quad \eta = 1 + \frac{80h_{air}}{h_{tot}} \Rightarrow h_{tot} = \frac{(k-1)h_{tot}}{80}$$

$$\text{thus } h_{tot} = \frac{h_{tot}}{80} \times \left(\frac{\frac{2V_{in}}{V_{out}} - 2 + \sqrt{\left(\frac{2V_{in}}{V_{out}} - 2 \right)^2 - 4}}{2} - 1 \right)$$

$$= \frac{h_{tot}}{80} \times \left(\frac{V_{in}}{V_{out}} + \sqrt{\frac{V_{in}}{V_{out}} - 1}^2 - 2 \right)$$


f) $vole(V_{out}) = vole(V_{in}) \times vole\left(\frac{C_{tot}(C_{air}) - vole(C_{water})}{(vole(C_{air}) + vole(C_{water}))^2}\right) = V \cdot \left(\frac{F \cdot F}{F^2 + E^2} \right) = V \cdot \frac{F^2}{F^2 + E^2} = V_{out} \cdot \frac{F^2}{F^2 + E^2}$

$$\text{vole } h_{tot} = \frac{m}{80} \times \left(\frac{V_{in}}{V_{out}} + \sqrt{\frac{V_{in}}{V_{out}} - 1}^2 - 2 \right) \Rightarrow \frac{m}{80} \times \left(1 + \sqrt{\left(\frac{V_{in}}{V_{out}} - 1 \right)^2 - 1} \right) \Rightarrow m \Rightarrow \text{meters.}$$

```


function Vout = the_plot(heights)
    Vin = 12;
    w = 0.5;
    htot = 1;
    c = 8.854 * 1e-12;
    Cknown = c * htot;
    Vout = zeros(size(heights));
    for i = 1:length(heights);
        height = heights(i);
        Ctank = c * (htot + 80 * height);
        Vout(i) = 2 * Vin * (Ctank * Cknown)/(Ctank + Cknown)^2;
    end
    plot(heights, Vout)
    xlabel('Heights of Water')
    ylabel('Vout')
end

```

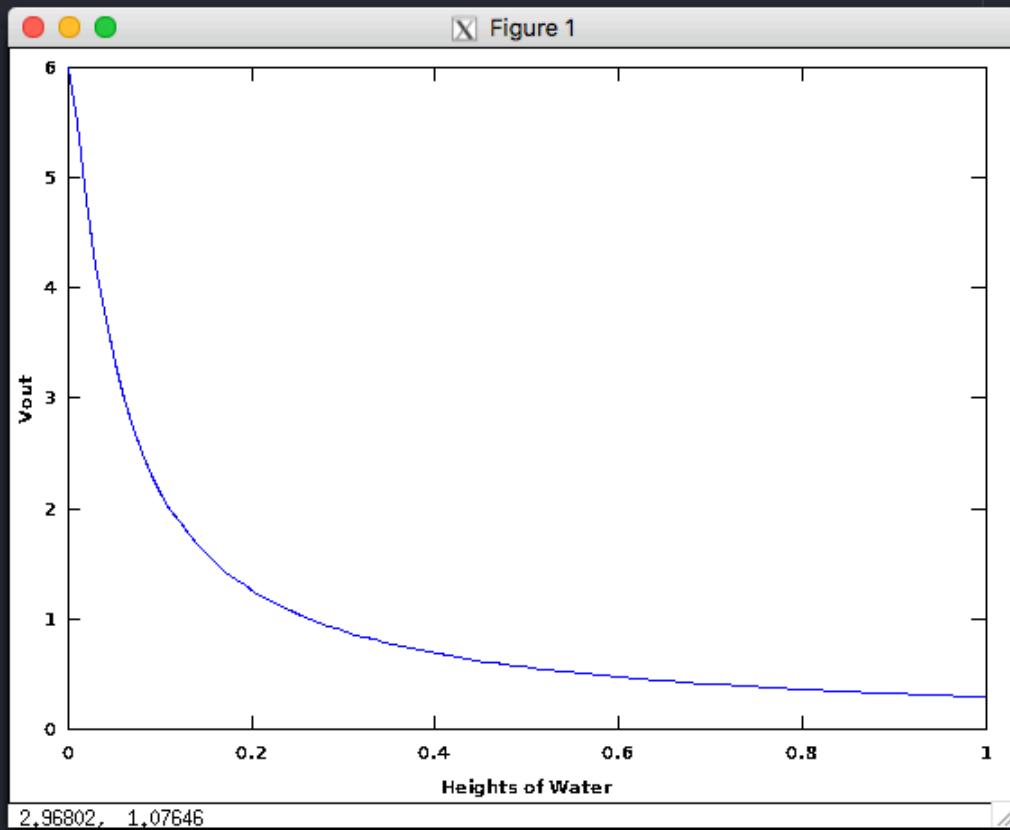

7. Cool for Summ.

a)

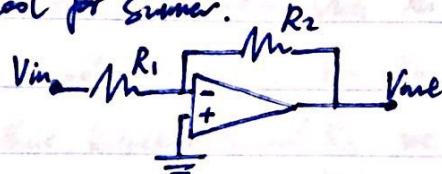


$$V_t = V_- = 0$$

$$\text{thus, } \frac{0 - V_{in}}{R_1} + \frac{0 - V_{out}}{R_2} = 0 \Rightarrow V_{out} = -\frac{R_2}{R_1} \cdot V_{in}$$

$$\text{Voltage gain: } \frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1}$$

b)

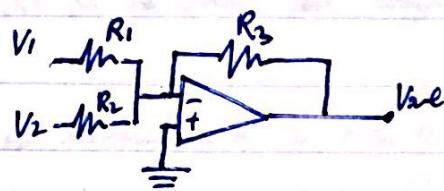

$$V_t = V_- = 0$$


$$\text{thus, } \frac{0 - V_1}{R_1} + \frac{0 - V_2}{R_2} + \frac{0 - V_{out}}{R_3} = 0$$

$$\text{thus } V_{out} = -R_3 \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} \right)$$

c) $V_{out} = -(\frac{1}{4}k_{s1} + 2k_{s2}) \Rightarrow \frac{R_3}{R_1} = \frac{1}{4} \Rightarrow \frac{R_3}{R_2} = 2.$

Thus, possibly, $R_3 = 1k\Omega$. thus $R_1 = 4k\Omega$. thus $R_2 = 500\Omega$.

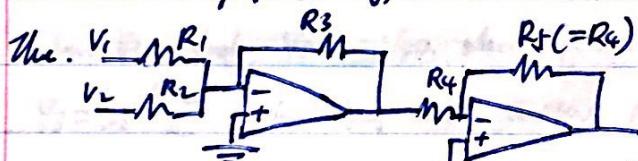d) Since the first op-amp is an inverting amplifier, thus V_{out} is negative. thus we need to add another amplifier (inverter) to blame it back.



The signs are inverted, but the value of V_{out} do not change if we add the other op-amp.

$$\text{thus gain} = \frac{V_{out}}{V_{in2}} = -1 \Rightarrow |g_{out}| = 1$$

$$\text{thus } \frac{V_{out}}{V_{in2}} = -\frac{R_f}{R_4} = -1 \Rightarrow R_f = R_4$$

8. Wheless Communication with an LED.

a) By Gohlin Rule: $V = V_+$. Thus $V_0 = V_2 = 0$, and since there's no current between V_0 and V_- thus, between R_1 and R_2 , we have $\frac{V_1}{R_1} \xrightarrow{I_1} \frac{V_2}{R_2} \xrightarrow{I_2} 0V$, and $V_1 \neq 0$
 Thus $|I_1| = \left| \frac{V_1}{R_1} \right|$, $|I_2| = \left| \frac{V_2}{R_2} \right|$. when $R_1 = R_2$, the value of $i_1 = i_2$, if not then $i_1 \neq i_2$
 and as no current pass through V_+ and V_- , $I_S = i_1$, $i_2 = i_3$ (if we take the direction of I counter, then $i_1 \neq i_3$ anyways)

b) As discussed in a), by Gohlin Rule, $V_0 = V_2 = 0$, and $i_1 = \frac{0 - V_1}{R_1} = -\frac{V_1}{R_1}$
 thus $V_1 = -i_1 R_1$, and $i_3 = \frac{V_2 - V_3}{R_3} \Rightarrow V_3 = -i_3 R_3 + V_2 = -i_3 R_3 = -i_2 R_3 = -R_3 \left(\frac{V_1 - V_2}{R_2} \right)$
 $= -R_3 \frac{V_1}{R_2} = -R_3 \frac{-I_S R_1}{R_2} = \frac{I_S R_1 R_3}{R_2}$

c) Same as problem [6]. we can check units.

$$u(V) = -(A) \cdot (R) = u(V_s) \text{ [correct]}.$$

$$u(dV) = 0 \text{ vols [correct]} \quad V_3 = \frac{(A)(R)(dV)}{C(R)} = dV_s \text{ [correct]}$$

d) when $V_3 > V_{ref}$, $V_{out} = V_{DD}$. when $V_{ref} > V_3$, $V_{out} = V_{SS}$


$$V_3 = I_S \frac{R_1 R_3}{R_2}, \text{ since } V_{ref} = 2V, R_1 = 10\Omega, R_2 = 100\Omega, I_S = 0 \text{ or } 0.1A$$

when $I_S = 0A$, then $V_3 = 0V$, then $V_{out} = V_{SS} = -5V$

$$\text{when } I_S = 0.1A, \text{ then } V_3 = 0.1 \times \frac{10 \times R_3}{1000} = 0.01R_3,$$


in order to get $V_{out} = V_{DD}$, $V_3 > V_{ref} \Rightarrow 0.01R_3 > 2 \Rightarrow R_3 > 200\Omega$

thus we can for example set $R_3 = 300\Omega$.

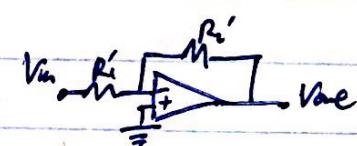e) ~~We can check the units~~ $V_3 = -\frac{R_3}{R_2} V_1$ 

Since O_1 and O_2 are inverters, we must ensure that for small or large
 Some input, we ~~can~~ can amplify the input be larger than R_{ref} . we leave we can amplify
 it. thus $|V_3| > |V_1|$, thus $R_3 > R_2$, and it works.

9. DC-DC Voltage Divider

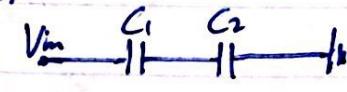a) Simplify the circuit: 

$$Q_1 = Q_2 = V_1 C_1 = V_2 C_2 \Rightarrow Q_{\text{total}} = Q_1 = Q_2 = C_{\text{total}} \cdot V_{\text{in}} = \left(\frac{1}{C_1} + \frac{1}{C_2}\right)^{-1} V_{\text{in}} = V_{\text{in}} \frac{C_1 C_2}{C_1 + C_2}$$

$$\text{thus } C_1 = \frac{Q_1}{V_1} = \frac{V_{\text{in}} C_1 C_2}{(C_1 + C_2) V_1}, \quad C_2 = \frac{V_{\text{in}} C_1 C_2}{(C_1 + C_2) V_2} \quad C_{\text{total}} = \frac{C_1 C_2}{C_1 + C_2}$$

$$\left. \begin{array}{l} V_1 + V_2 = V_{\text{in}} \\ V_1 C_1 = Q_1 = Q_{\text{total}} = V_{\text{in}} \frac{C_1 C_2}{C_1 + C_2} \Rightarrow V_1 = V_{\text{in}} \frac{C_2}{C_1 + C_2} \\ V_2 C_2 = Q_2 = \dots \end{array} \right\} \Rightarrow V_2 = V_{\text{in}} \frac{C_1}{C_1 + C_2}$$

$$b) Q_{\text{total}}^2 = Q_1 + Q_2 = 2 \times Q_{\text{total}} = 2 V_{\text{in}} \frac{C_1 C_2}{C_1 + C_2} = V_{\text{out}} \times C_{\text{total}}^2 = V_{\text{out}} \times (C_1 + C_2)$$

$$\text{thus } V_{\text{out}} = 2 V_{\text{in}} \frac{C_1 C_2}{(C_1 + C_2)^2}$$

$$c) \text{when } C_1 = C_2, \quad V_{\text{out}} = 2 V_{\text{in}} \frac{C_1^2}{(2 C_1)^2} = \frac{1}{2} V_{\text{in}}$$

$$\text{Phase 1: } Q_{\text{total}} = V_{\text{in}} \frac{C_1 C_2}{C_{\text{total}}}, \quad E_1 = \frac{1}{2} C V^2 = \frac{1}{2} \times C_{\text{total}} V_{\text{in}}^2 = \frac{1}{2} \times \frac{C_1}{2} \cdot V_{\text{in}}^2 = \frac{C_1}{4} V_{\text{in}}^2$$

$$C_{\text{total}} = \frac{C_1 C_2}{C_{\text{total}}} = \frac{C_1}{2}$$

$$\text{Phase 2: } E_2 = \frac{1}{2} C V^2 = \frac{1}{2} \times (C_1 + C_2) \times \left(\frac{1}{2} V_{\text{in}}\right)^2 = \frac{C_1}{4} V_{\text{in}}^2$$

$$\epsilon = \frac{E_2}{E_1} = 100\%$$

10. Fansheng Cheng: 3033207858

Samuel Harreschau: 23804699

Cong Yang: 3032217722