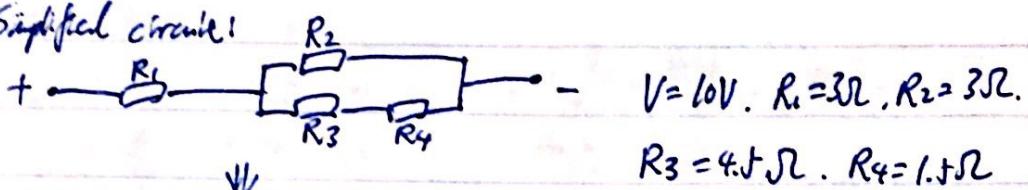


Homework #4.

1. Mechanical Circuits

Simplified circuit:




$$V = 10V, R_1 = 3\Omega, R_2 = 3\Omega,$$

$$R_3 = 4.5\Omega, R_4 = 1.5\Omega$$

$$\text{Total } R = R_1 + \left(\frac{1}{R_2} + \frac{1}{R_3 + R_4} \right)^{-1} = 3\Omega + \left(\frac{1}{3} + \frac{1}{6} \right)^{-1} = 5\Omega$$
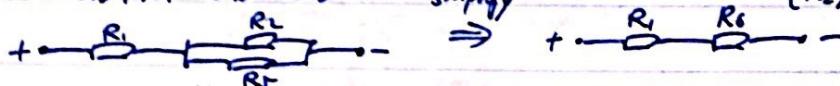
$$\text{Let } R_3 + R_4 = R_5 = 6\Omega \quad \text{simplify} \quad (R_2/R_5)_{\text{series}} = R_5 = 2\Omega$$



$$\text{For } R_1: I_1 = \frac{V}{R_{\text{total}}} = \frac{10V}{5\Omega} = 2A, V_1 = \frac{R_1}{R_1 + R_5} \cdot V = \frac{3}{3+2} \times 10 = 6V$$

$$\text{For } R_2: I_2 = \frac{R_1}{R_1 + R_2}, I_1 = \frac{6}{9} \cdot 2A = \frac{4}{3}A, V_2 = \frac{R_2}{R_{\text{total}}} \cdot V = \frac{2\Omega}{5\Omega} \cdot 10V = 4V$$

$$\text{For } R_3: I_3 = \frac{R_2}{R_2 + R_3} \cdot I_1 = \frac{3}{9} \cdot 2A = \frac{2}{3}A, V_3 = \frac{R_3}{R_3 + R_4} \cdot V_2 = \frac{4.5}{6} \times 4V = 3V$$

$$\text{For } R_4: I_4 = I_3 = \frac{2}{3}A, V_4 = \frac{R_4}{R_4 + R_5} V_2 = \frac{1.5}{6} \times 4V = 1V$$

2. Cell Phone Battery.

$$a) Q = It \Rightarrow t = \frac{Q}{I} = \frac{2770 \text{ mAh}}{0.4 \text{ A}} = 26.3 \text{ h}$$

$$b) 1 \text{ Ah} = 3600 \text{ As} = 3.6 \text{ C} \Rightarrow 2770 \text{ mAh} = 2770 \times 3.6 \text{ C} = 9972 \text{ C}$$

$$\# \text{ of Electrons} = 9972 \text{ C} / 1.602 \times 10^{-19} = 6.2247 \times 10^{22} \text{ electrons}$$

$$c) W = Pt = 0.4 \text{ W} \cdot 26.3 \text{ h} \times 3600 \text{ s/h} = 37893.6 \text{ J}$$

$$d) \text{Cost} = W_{\text{real}} \times 0.16 \$/\text{kWh} = 37893.6 \text{ J} / 3600 \text{ s/h} \times 3 \times 0.16 \$/\text{kWh} \approx \$0.0522$$

$$e) P_{\text{real}} = \frac{V^2}{R} = \left(\frac{R_{\text{real}}}{2(R_{\text{real}} + R_{\text{bat}}) \times 5\Omega} \right)^2 / R_{\text{real}} = \left[\frac{2t R_{\text{real}}}{(2000\Omega + R_{\text{real}})^2} \right] W$$

$$\textcircled{1} R_{\text{bat}} = 1 \text{ m}\Omega, P_{\text{real}} = \frac{2t \times 1 \text{ m}\Omega}{(200 \times 10^3 \text{ m}\Omega)^2} = 0.6188 \text{ W}, t = \frac{37893.6 \text{ J}}{0.6188} \approx 17 \text{ h}$$

$$\textcircled{2} R_{\text{real}} = 1 \Omega, P_{\text{real}} = \frac{2t \times 1 \Omega}{(1.2)^2} = 17.36 \text{ W}, t = \frac{37893.6 \text{ J}}{17.36} \approx 2182 \text{ seconds}$$

$$\textcircled{3} R_{\text{real}} = 10 \text{ k}\Omega, P_{\text{real}} = \frac{2t \times 10^4}{(10000 \cdot 1)^2} \approx 2t \times 10^{-4} \text{ W}, t = \frac{37893.6 \text{ J}}{0.00025} = 15153046 \text{ s} \approx 175 \text{ days}$$

3. Nodal Analysis

a) KCL for Node 1 & 2

$$\textcircled{1} \quad I - \frac{V_1}{R_1} - \frac{V_1 - V_2}{R_2} = 0$$

$$I - \frac{V_1}{10} - \frac{V_1 - V_2}{20} = 0$$

$$20 - 3V_1 + V_2 = 0$$

$$3V_1 - V_2 = 20$$

$$\begin{bmatrix} 3 & -1 \\ -7 & 1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 20 \\ 100 \end{bmatrix}$$

$$\textcircled{2} \quad \frac{V_1 - V_2}{R_2} + \frac{0 - V_2}{R_3} + (-3) = 0$$

$$\frac{V_1 - V_2}{20} + \frac{-V_2}{50} = 3$$

$$5V_1 - 5V_2 - 2V_2 = 300$$

$$5V_1 - 7V_2 = 300$$

$$\begin{bmatrix} 3 & -1 \\ -7 & 1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 20 \\ 300 \end{bmatrix} \Rightarrow \begin{bmatrix} 16 & 0 \\ -7 & 3 \end{bmatrix} \Rightarrow \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} -10 \\ -50 \end{bmatrix}$$

$$\Rightarrow \text{Thus } V_1 = -10V \quad V_2 = -50V$$

Verification by superposition.

Loop A (clockwise "IA" current on left) Loop B ("3A" on the right)

(denote current pass $R_1 \Rightarrow I_1$, $R_3 \Rightarrow I_3$)

Thus Loop A ($I_A = 1A$)

$$I_1^A = \frac{R_2 + R_3}{R_1 + R_2 + R_3} \cdot I_A$$

$$= \frac{50}{80} \cdot 1A = 0.625A$$

$$I_3^A = I_A - I_1^A = 0.125A$$

$$V_{1A} = I_1^A \cdot R_1 = 0.625 \cdot 10\Omega = 6.25V$$

$$V_{3A} = I_3^A \cdot R_3 = 0.125 \cdot 50\Omega = 6.25V$$

Loop B ($I_B = 3A$)

$$I_1^B = \frac{R_3}{R_1 + R_2 + R_3} \cdot I_B$$

$$= \frac{50}{80} \cdot 3A = 1.875A$$

$$I_3^B = I_B - I_1^B = 1.125A$$

$$V_{1B} = I_1^B \cdot R_1 = 0.625A \cdot 10\Omega = 6.25V$$

$$V_{3B} = I_3^B \cdot R_3 = 1.125A \cdot 50\Omega = 56.25V$$

Set direction of I_A as positive direction

$$\text{Then } V_1 = V_{1A} - V_{1B} = 6.25V - 6.25V = -10V$$

$$V_2 = V_{2A} - V_{2B} = 6.25V - 56.25V = -50V$$

\Rightarrow same as the previous answer.

b) KCL for node 1 & 2

$$\textcircled{1} \frac{V_1}{R_1} + \frac{V_L}{R_2} + \frac{V_1 - V_2 - 10V}{R_3 + R_4} - 10V_1 = 0$$

$$\frac{V_1}{10} + \frac{V_L}{10} + \frac{V_1 - V_2 - 10}{105} - 10V_1 = 0$$

$$\textcircled{2} \frac{V_2 - V_1 + 10V}{R_3 + R_4} + \frac{V_2}{R_f} = 0$$

$$\frac{V_2 - V_1 + 10}{105} + \frac{V_2}{60} = 0$$

From the note for V_1 , and since one side of V_2 is ground-connected. $V_2 = V_T$

$$\textcircled{1} 10V_1 + 10V_2 + 10V_1 - 10V_2 - 100 - 10V_0 + V_2 = 0$$

$$110V_1 - 1040 + V_2 = 100$$

$$\textcircled{2} 60V_2 - 60V_1 + 600 + 10V_2 = 0$$

$$60V_1 - 16V_2 = 600$$

$$\left\{ \begin{bmatrix} 110 & -1040 \\ 60 & -16 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 100 \\ 600 \end{bmatrix} \right.$$

$$\Downarrow V_1 \approx 10.2862 \text{ V}$$


$$V_2 \approx 0.10408 \text{ V}$$

$$I = \frac{V_1}{R_1} = 3 \text{ A}$$

$$R = \frac{V_2}{I} = 3 \cdot 8$$

4. Thévenin and Norton Equivalent Circuits


a) Simplify the circuit:

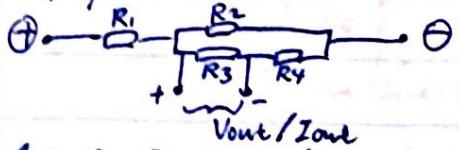

$$R_1 = 3\Omega, R_2 = 3\Omega, R_3 = 4\Omega, R_4 = 1.5\Omega, V = 10V$$

let $R_T = R_3 + R_4$ and R_S = the $R_1/R_2/R_3/R_4$ system, then $R_T = 6\Omega$, $R_S = \left(\frac{1}{R_1} + \frac{1}{R_2}\right)^{-1} = 2\Omega$

Rewrite the circuit

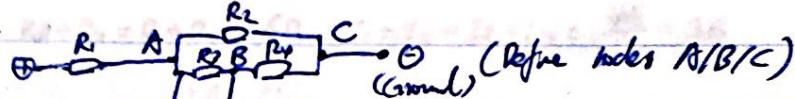

$$\text{Thus } V_{AB} = \frac{R_3}{R_T} \times V_{AC} = \frac{R_3}{R_T} \times \frac{R_4}{R_1 + R_2} \times V = \frac{4}{6} \times \frac{2}{3+2} \times 10 = 3V = V_{out} \text{ (Some Circles)}$$


$$I_{AB} = I_4 = \frac{V_{AC'}}{R_4} \Rightarrow R'_S = \left(\frac{1}{R_1} + \frac{1}{R_2}\right)^{-1} = \left(\frac{1}{3} + \frac{1}{1.5}\right)^{-1} = 1\Omega \Rightarrow V_{AC'} = \frac{R'_S}{R_1 + R_2} \times 10V = 2.5V \text{ (short } R_3)$$

$$= 2.5V / 4\Omega = \frac{5}{8}A = I_{out}$$

$$R_{out} = \frac{V_{out}}{I_{out}} = \frac{3V}{\frac{5}{8}A} = \frac{9}{5}\Omega$$

Thus:


Thévenin equivalent circuit \Rightarrow

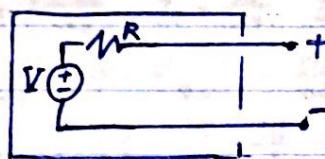

$$V = V_{out} = 3V$$

$$R = R_{out} = \frac{9}{5}\Omega$$

Norton equivalent circuit \Rightarrow

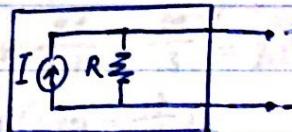

$$I = I_{out} = \frac{5}{8}A$$

$$R = R_{out} = \frac{9}{5}\Omega$$


$$V = V_{out} = 3V$$

$$R = R_{out} = \frac{9}{5}\Omega$$

$$I_{out} = 2.5A$$

$$R_{out} = 1.8\Omega$$

b) Simplify the circuit:

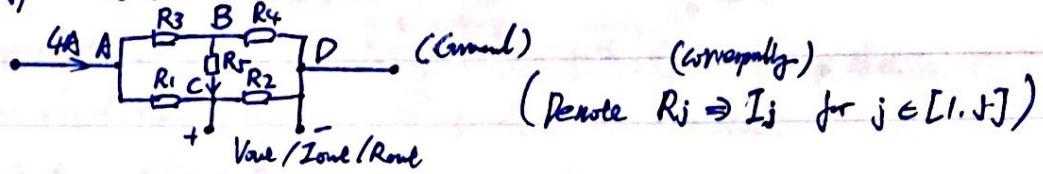

Thus we have $I = 4A$, $R_1 = 4\Omega$, $R_2 = 1\Omega$, $R_3 = 4\Omega$, $R_4 = 1\Omega$, $R_5 = 3\Omega$

By symmetry, since $R_3 + R_4 = R_1 + R_2 = 6\Omega$, $I_1 = I_2 = I_3 = I_4 = \frac{6A}{2} = 3A$.

$$\text{Thus } V_{out} = I_2 \cdot R_2 = V_2 = 2A \cdot 1.5\Omega = 3V$$

Now short $R_2 \Rightarrow$ Create same as

The circuit diagram shows a bridge network with four resistors labeled R_1 , R_2 , R_3 , and R_4 . A dependent current source, labeled ctrl , is connected between node C and ground. The output voltage V_P is measured across resistor R_4 .

And we have : Mode A: $4A - I_3 - I_1 = 0$

$$\text{Node B: } I_3 - I_9 - I_4 = 0 \quad \text{Node C: } I_1 + I_5 - I_{\text{out}} = 0$$

$$I_1 = \frac{V_A}{R_1}, \quad I_3 = \frac{V_A - V_B}{R_3}, \quad I_4 = \frac{V_B}{R_4}, \quad I_T = \frac{V_B}{R_T}$$


$$\text{Thus } \begin{cases} 4 - \frac{V_A - V_B}{R_3} - \frac{V_A}{R_1} = 0 \\ \frac{V_A - V_B}{R_3} - \frac{V_B}{R_4} - \frac{V_B}{R_5} = 0 \end{cases} \Rightarrow \begin{cases} 4 - \frac{V_A - V_B}{4.5} - \frac{V_A}{4.5} = 0 \\ \frac{V_A - V_B}{4.5} - \frac{V_B}{1.5} - \frac{V_B}{3} = 0 \end{cases} \Rightarrow \begin{cases} V_A = 9.9V \\ V_B = 1.8V \end{cases}$$

$$\text{Thus } I_{\text{out}} = I_1 + I_2 = \frac{V_A}{R_1} + \frac{V_B}{R_2} = \frac{9.9}{4.5} + \frac{1.8}{3} = 2.2 + 0.6 = 2.8A$$

$$\text{Thus } R_{\text{out}} = V_{\text{out}} / I_{\text{out}} = 3V / 2.8A = \frac{11}{14} \Omega$$

Thru


Thevenin equivalent circuit

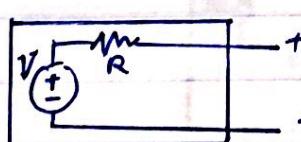

$$V = V_{out} = 32$$

$$R = R_{\text{out}} = \frac{15}{14} r$$

Norton equivalent circuit

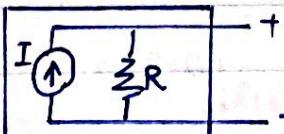

$$I = I_{out} = 2.8A$$

$$R = R_{\text{out}} = \frac{1}{14} n$$

5. Nodal Analysis Or Superposition?

Simplify the circuit:

And define nodes

$$\text{Node A: } i + I_E = 1A ; V_{ED} = 5V \Rightarrow V_E = 5V.$$

$$V_{AB} = V_{CD} = 1.5\Omega \cdot 1A = 1.5V$$

For current $i \Rightarrow$ since $1.5\Omega + 1.5\Omega = 3\Omega$. it is dual equally to Path 2/3.

$$\text{And since } V_{AD} = V_{AO} \Rightarrow ((1A - \frac{i}{2}) \times 1.5\Omega + 1.5\Omega) = -(3\Omega(-i) - \frac{i}{2}) \times 3\Omega \Rightarrow i = -\frac{1}{3}A$$

$$i + I_E = 1A \quad \left(\frac{V_{DA}}{3\Omega} + \frac{5V}{3\Omega} + \frac{V_{AD}}{3\Omega} = 1A \right) \Rightarrow V_{AD} = -1V \Rightarrow i = \frac{V_{AD}}{3\Omega} = -\frac{1}{3}A$$


Solve and we get $i = -\frac{1}{3}A$

6. Thermistor

a) Simplify the original circuit: V_{bt}

$$V_{out} = V_A - V_B = V_b \left(\frac{R_3}{R_2 + R_3} \right) - V_b \left(\frac{R_2}{R_1 + R_2} \right)$$

Then, Thevenin equivalent circuit:

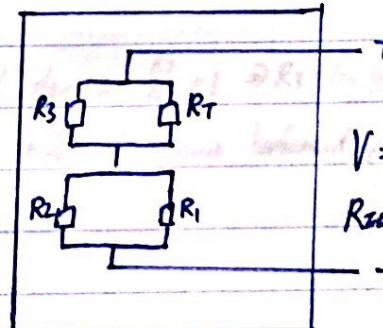

$$V = V_{out}$$

$$R_{thev} = \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} + \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1}$$

$$b) V_o = V_{out} = V_b \left(\frac{R_3}{R_1 + R_2} \right) - V_b \left(\frac{R_2}{R_1 + R_2} \right)$$

$$V_b(R_3(R_1+R_2) - R_2(R_1+R_2)) = V_b(R_1+R_2)(R_1+R_2)$$

$$\frac{V_b R_2 (R_1+R_2)}{R_1+R_2} = V_b(R_1+R_2) + V_b R_2 \Rightarrow R_1 = \frac{V_b R_3 (R_1+R_2) - V_b (R_1+R_2) R_2 - V_b R_2 R_3}{V_b (R_1+R_2) + V_b R_2}$$

$$= R_3 \frac{V_b R_1 - V_b (R_1+R_2)}{V_b R_2 + V_b (R_1+R_2)}$$

- c) If $R_T = R_1 = R_2 = R_3$, by symmetry, $V_{AB} = V_{out} = V_0 = 0$. if Temperature T rise, R_T decreases.
 Then, $V_b \left(\frac{R_2}{R_T + R_3} \right) - V_b \left(\frac{1}{2} \right) > 0$, which means $V_{AB} = V_{out} = V_0 > 0V$
 If Temperature \downarrow decrease, R_T increase \uparrow , thus, $\frac{R_2}{R_T + R_3} < \frac{1}{2}$, thus, $V_{AB} = V_{out} = V_0 < 0V$

d) $R_T(T) = R(T_0) \exp(\beta \left(\frac{1}{T} - \frac{1}{T_0} \right))$, $Q = \frac{dV_b}{dT} = R_T \frac{dV_b}{dR_T} \frac{1}{R_T} \frac{dR_T}{dT}$

$$\frac{dR_T(T)}{dT} = -\beta \times \frac{1}{T^2} \times R(T_0) \exp(\beta \left(\frac{1}{T} - \frac{1}{T_0} \right)) = \frac{-\beta}{T^2} R_T$$

$$V_0 = V_b \left(\frac{R_2}{R_T + R_3} - \frac{R_2}{R_1 + R_2} \right) \Rightarrow \frac{dV_0}{dR_T} = \frac{-V_b R_3}{(R_3 + R_T)^2}$$

$$Q = R_T \frac{dV_0}{dR_T} \frac{1}{R_T} \frac{dR_T}{dT} = \frac{-V_b R_3 R_T}{(R_3 + R_T)^2} \times \frac{-\beta}{T^2} \Rightarrow \lambda = \frac{R_3}{R_T} = \frac{V_b \alpha \beta}{(1+\alpha)^2 T^2}$$

$$\frac{dQ}{d\lambda} = 0 = \frac{d}{d\lambda} \left(\frac{V_b \beta}{T^2} (1+\alpha)^{-1} \left(\frac{1}{\lambda} + 1 \right)^{-1} \right) = \frac{V_b \beta}{T^2} \left(-\frac{1}{(1+\alpha)^2} \frac{2}{\lambda^2} + \frac{1}{(1+\alpha)} \frac{\frac{1}{\lambda^2}}{(1+\alpha)^2} \right)$$

$$= \frac{V_b \beta}{T^2} \left(-\frac{2}{(1+\alpha)^3} + \frac{1}{1+\alpha} \cdot \left(\frac{1}{\alpha^2} \times \frac{\beta^2}{(1+\alpha)^2} \right) \right) = \frac{V_b \beta}{T^2} \times \frac{(1-\alpha)}{(1+\alpha)^3} = 0$$


thus $\lambda = 1$ if $\frac{dQ}{d\lambda} = 0$

e) $R_T = 3.4k\Omega$ when $T = 30^\circ C$.

Since $\frac{dQ}{d\lambda} = \frac{V_b \beta}{T^2} \frac{(1-\alpha)}{(1+\alpha)^3} = 0$ is max, and then $\lambda = \frac{R_3}{R_T} = 1 \Rightarrow R_3 = R_T = 3.4k\Omega$ (while $R_2 = R_1$)


Now $R_2 = R_3 = R_T$, we can set $R_1 = R_2$ to make the circuit balanced, thus $V_0 = 0V$ and can show variance in a more clear way.

thus,

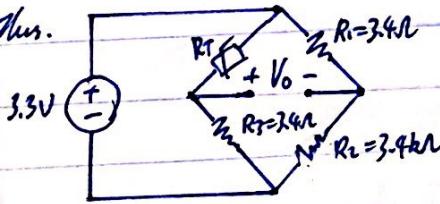

7. Multitouch Resistive Touchscreen.

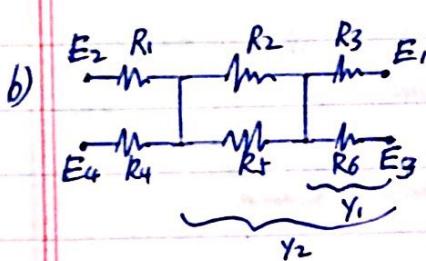a) $R = \rho \frac{L}{A} = \rho \left(\frac{L}{T \cdot W} \right) = 1 \times \left(\frac{0.12}{0.03 \times 0.005} \right) = 8 \times 10^3 \Omega = R_{E12}$



$$R_1 = R_4 = \frac{12 - Y_2}{12} \times R_{E12} = \frac{1}{12} \times 5 \approx 2.0833 \text{ k}\Omega$$

$$R_2 = R_5 = \frac{Y_2 - Y_1}{12} \times R_{E12} = \frac{2-3}{12} \times 5 \approx 1.6667 \text{ k}\Omega$$

$$R_3 = R_6 = \frac{Y_1}{12} \times R_{E12} = \frac{3}{12} \times 5 = 1.25 \text{ k}\Omega$$

c) Thus $R_{\text{real}} = R_4 + \left(\frac{1}{R_2} + \frac{1}{R_5} \right)^{-1} + R_6 = 2.0833 + \left(\frac{1}{1.6667} + \frac{1}{1.6667} \right)^{-1} + 1.25 \approx 4.1667 \text{ k}\Omega$

Thus $V_{Q3} = R_{\text{real}} \times 1 \text{ mA} = 4.1667 \times 10^3 \times 1 \times 10^{-3} \approx 4.1667 \text{ V}$

d) $R_1 = R_4 = \frac{12 - Y_2}{12} R_{E12} = \frac{12 - Y_2}{12} \times 5 \text{ (k}\Omega\text{)} \quad R_2 = R_5 = \frac{Y_2 - Y_1}{12} \times 5 \text{ (k}\Omega\text{)} \quad R_3 = R_6 = \frac{Y_1}{12} \times 5 \text{ (k}\Omega\text{)}$

$$\text{Thus } R_{Q3} = R_4 + \left(\frac{1}{R_2} + \frac{1}{R_5} \right)^{-1} + R_6 = \frac{12 - Y_2}{12} \times 5 + \left(\frac{12 - X_2}{5 \times (Y_1 - Y_2)} \right)^{-1} + \frac{Y_1}{12} \times 5 \\ = \frac{5}{12} \left(12 - Y_2 + \frac{Y_1 - Y_2}{2} + Y_1 \right) = \frac{5}{12} \left(\frac{1}{2} Y_1 - \frac{1}{2} Y_2 + 12 \right) \text{ (k}\Omega\text{)}$$

Thus $V_{Q3} = R_{Q3} \cdot 1 \text{ mA} = \frac{5}{12} \left(\frac{1}{2} Y_1 - \frac{1}{2} Y_2 + 12 \right) \text{ V}$, thus we can decouple V_{E4-E3} by measuring Y_1 and Y_2 .

e) $V_{E4-E2} = 1 \text{ mA} \times R_4 = 1 \times 10^{-3} \times \frac{12 - Y_2}{12} \times 5 \times 10^3 = \frac{12 - Y_2}{12} \times 5 \text{ (V)}$

$$V_{E1-E3} = 1 \text{ mA} \times R_6 = 1 \times 10^{-3} \times \frac{Y_1}{12} \times 5 \times 10^3 = \frac{Y_1}{12} \times 5 \text{ (V)}$$

8. SPICE-y Circuits

(a) Simplify circuit:

$$\text{The } F = \begin{bmatrix} & & & & & \\ & & & & & \\ & & & & & \\ & & & & & \\ & & & & & \\ & & & & & \end{bmatrix} \xrightarrow{\text{row: currents}} \begin{bmatrix} 1 & -1 & 0 & 0 & 0 & \\ 0 & 1 & 0 & -1 & 0 & \\ 0 & 0 & 1 & 0 & 0 & \\ 0 & 0 & 0 & 1 & 0 & \\ 0 & 0 & 0 & 0 & 1 & \\ 0 & 0 & 0 & 0 & 0 & 1 \end{bmatrix} \xrightarrow{\text{column balance of nodes}} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ I_S \end{bmatrix}$$

(Without independent source)
(Take input as (-1) and output as (1))

$$F(\text{with independent source}) = \begin{bmatrix} 1 & -1 & 0 & 0 & 0 & \\ 0 & 1 & 0 & -1 & 0 & \\ 0 & 0 & 1 & 0 & 0 & \\ 0 & 0 & 0 & 1 & 0 & \\ 0 & 0 & 0 & 0 & 1 & \\ 0 & 0 & 0 & 0 & 0 & 1 \end{bmatrix} \begin{cases} i_{1S} \\ i_{2S} \\ i_{3S} \\ i_{4S} \\ i_{5S} \\ I_S \end{cases}$$

(b) $\tilde{F}^T \tilde{i} = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & -1 & 0 \\ -1 & 1 & 1 & 0 & 0 & 0 & 0 \\ 0 & -1 & 0 & 1 & 0 & 0 & -1 \\ 0 & 0 & -1 & -1 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & -1 & 1 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ I_S \\ I_{1S} \end{bmatrix} = \begin{bmatrix} i_1 - I_{1S} \\ -i_1 + i_2 + i_3 \\ -i_2 + i_4 - I_{1S} \\ -i_3 - i_4 + i_5 \\ -i_4 + I_{1S} + I_S \\ I_S \end{bmatrix} \Rightarrow \text{This shows the KCL equations at each node}$

(c) $\tilde{F}^T \tilde{v} = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & -1 \\ -1 & 1 & 1 & 0 & 0 & 0 \\ 0 & -1 & 0 & 1 & 0 & 0 \\ 0 & 0 & -1 & -1 & 1 & 0 \\ 0 & 0 & 0 & 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ I_{1S} \end{bmatrix} = \begin{bmatrix} i_1 - I_{1S} \\ -i_1 + i_2 + i_3 \\ -i_2 + i_4 - i_5 \\ -i_3 - i_4 + i_5 \\ -i_4 + I_{1S} \\ I_{1S} \end{bmatrix} = -I_S \begin{bmatrix} 0 \\ 0 \\ -1 \\ 0 \\ 1 \\ 0 \end{bmatrix}$

(d) $F \cdot \vec{u} = \begin{bmatrix} 1 & -1 & 0 & 0 & 0 \\ 0 & 1 & -1 & 0 & 0 \\ 0 & 0 & 1 & -1 & 0 \\ 0 & 0 & 0 & 1 & -1 \\ 0 & 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} u_1 \\ u_2 \\ u_3 \\ u_4 \\ u_5 \end{bmatrix} = \begin{bmatrix} u_1 - u_2 \\ u_2 - u_3 \\ u_3 - u_4 \\ u_4 - u_5 \\ u_5 - u_1 \end{bmatrix} = \vec{v}$ Correspond to $R_1 \sim R_5$ (the voltage across which)

correspond to V_S (the voltage across which)

correspond to I_S (the voltage across which)

(e) $\vec{d} = \vec{v} = \begin{bmatrix} i_1 \cdot R_1 \\ i_2 \cdot R_2 \\ i_3 \cdot R_3 \\ i_4 \cdot R_4 \\ i_5 \cdot R_5 \\ V_S \\ V_{C1} \end{bmatrix}$

$$f) \vec{d} = R\vec{i} + \vec{V}_S = \begin{bmatrix} R_1 & 0 & 0 & 0 & 0 & 0 \\ 0 & R_2 & 0 & 0 & 0 & 0 \\ 0 & 0 & R_3 & 0 & 0 & 0 \\ 0 & 0 & 0 & R_4 & 0 & 0 \\ 0 & 0 & 0 & 0 & R_5 & 0 \\ 0 & 0 & 0 & 0 & 0 & V_{CS} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ V_E \end{bmatrix} = \begin{bmatrix} hR_1 \\ hR_2 \\ hR_3 \\ hR_4 \\ hR_5 \\ V_{CS} \end{bmatrix}$$

$$F_U - R\vec{i} = \vec{V}_S = \begin{bmatrix} 1 & -1 & 0 & 0 & 0 & 0 \\ 0 & 1 & -1 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} u_1 \\ u_2 \\ u_3 \\ u_4 \\ u_5 \\ u_6 \end{bmatrix} - \begin{bmatrix} R_1 & R_2 & R_3 & R_4 & R_5 & 0 \\ 0 & 0 & 0 & 0 & 0 & 10 \end{bmatrix} \begin{bmatrix} h \\ h \\ h \\ h \\ h \\ 10 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ -V_S \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ V_{CS} \end{bmatrix}$$

$$g) A\vec{x} = \vec{b} = \begin{bmatrix} F - R \\ 0 & F^T \end{bmatrix} \begin{bmatrix} \vec{u} \\ \vec{i} \end{bmatrix}$$

$$\begin{bmatrix} 1 & -1 & 0 & 0 & -R_1 & 0 & 0 & 0 & 0 \\ 0 & 1 & -1 & 0 & 0 & -R_2 & 0 & 0 & 0 \\ 0 & 0 & 1 & -1 & 0 & 0 & -R_3 & 0 & 0 \\ 0 & 0 & 0 & 1 & -1 & 0 & 0 & -R_4 & 0 \\ 0 & 0 & 0 & 0 & 1 & -1 & 0 & 0 & -R_5 \\ 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} u_1 \\ u_2 \\ u_3 \\ u_4 \\ u_5 \\ u_6 \\ u_7 \\ u_8 \\ u_9 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$h) \hat{A}\hat{x} = \vec{b}$$

$$\begin{bmatrix} 1 & -1 & 0 & 0 & -R_1 & 0 & 0 & 0 & 0 \\ 0 & 1 & -1 & 0 & 0 & -R_2 & 0 & 0 & 0 \\ 0 & 0 & 1 & -1 & 0 & 0 & -R_3 & 0 & 0 \\ 0 & 0 & 0 & 1 & -1 & 0 & 0 & -R_4 & 0 \\ 0 & 0 & 0 & 0 & 1 & -1 & 0 & 0 & -R_5 \\ 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} u_1 \\ u_2 \\ u_3 \\ u_4 \\ u_5 \\ u_6 \\ u_7 \\ u_8 \\ u_9 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$i) \begin{bmatrix} 1 & -1 & 0 & 0 & -R_1 & 0 & 0 & 0 & 0 \\ 0 & 1 & -1 & 0 & 0 & -R_2 & 0 & 0 & 0 \\ 0 & 0 & 1 & -1 & 0 & 0 & -R_3 & 0 & 0 \\ 0 & 0 & 0 & 1 & -1 & 0 & 0 & -R_4 & 0 \\ 0 & 0 & 0 & 0 & 1 & -1 & 0 & 0 & -R_5 \\ 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} u_1 \\ u_2 \\ u_3 \\ u_4 \\ u_5 \\ u_6 \\ u_7 \\ u_8 \\ u_9 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

j) Use Zoython to calculate

$$\begin{aligned} u_1 &= 5V \\ u_2 &= 14.6V \\ u_3 &= 21.2V \\ u_4 &= 15.6V \\ i_1 &= -2.4 \times 10^{-3}A \\ i_2 &= -2.2 \times 10^{-3}A \\ i_3 &= -2 \times 10^{-3}A \\ i_4 &= 2.8 \times 10^{-3}A \\ i_5 &= 2.6 \times 10^{-3}A \\ i_6 &= -2.4 \times 10^{-3}A \end{aligned}$$

9. Resistive Voltage "Regulator"

a) $V_{out} = \frac{R}{R+10k\Omega} = 4V \quad \frac{R}{10k\Omega} = \frac{4V}{6V} = 2 \quad R = 20k\Omega$

b) Let R' denote the system of R and $1k\Omega$. $R' = (\frac{1}{R} + \frac{1}{1k\Omega})^{-1} = \frac{20}{21} k\Omega$
 $V_{out} = \frac{R'}{R'+10k\Omega} \times 6V = \frac{\frac{20}{21}}{\frac{20}{21} + 10} \times 6 \approx 0.52174V$

c) Let R' denote $[R | 10k\Omega]$ system $R' = (\frac{1}{R} + \frac{1}{10k\Omega})^{-1} = \frac{50}{3} \Omega$
 $V_{out} = \frac{R'}{R'+10k\Omega} \times 6V = \frac{\frac{50}{3}}{\frac{50}{3} + 10} \times 6 = 3.75V$

d) $I_{short} = I_{AO} = \frac{6V}{R_1} = (6V)G_1, \quad V_{short} = \frac{R_2}{R_1 R_2} \times 6V = \frac{1}{G_1 + G_2} (6V) = \frac{G_1}{G_1 + G_2} (6V)$
 $R_{eff} = V_{short}/I_{AO} = \frac{G_1}{G_1 + G_2} (6V) \times \frac{1}{(6V)G_1} = \frac{1}{G_1 + G_2}$
 $G_{eff} = \frac{1}{R_{eff}} = G_1 + G_2$

e) $V_{out} = I_{AO} \times \frac{R_{eff}}{R_{eff} + R_e} \times R_e \quad G [3.8, 4.2]$
 $\frac{1}{I_{AO} R_e} \times \frac{R_{eff} + R_e}{R_{eff}} G \left[\frac{1}{G_2}, \frac{1}{G_1} \right] \Rightarrow 1 + \frac{R_e}{R_{eff}} G \left[\frac{I_{AO} R_e}{G_2}, \frac{I_{AO} R_e}{G_1} \right]$
 $R_{eff} G \left[\frac{R_2 R_e}{I_{AO} R_e - G_2}, \frac{3.8 R_e}{I_{AO} R_e - G_1} \right] \Rightarrow \left[\frac{4.2}{I_{AO} G_2}, \frac{3.8}{I_{AO} G_1} \right]$
 $G_{eff} G \left[\frac{I_{AO}}{4.2} G_2, \frac{I_{AO}}{3.8} G_1 \right]$

f) $G_{eff} = G_1 + G_2 \Rightarrow G_2 G \left[\frac{I_{AO}}{4.2} G_2 - G_2 - G_1, \frac{I_{AO}}{3.8} G_1 - G_1 - G_2 \right] \Rightarrow \left[\frac{3}{7} G_1 - G_2, \frac{11}{19} G_1 - G_2 \right]$

g) $R_2 G [1 \text{ kOhm}, 100 \text{ kOhm}]$

$$G_2 G \left[\frac{3}{7} G_1 - 1 \text{ mS}, \frac{11}{19} G_1 - 1 \text{ mS} \right]$$

$$G_2 G \left[\frac{3}{7} G_1 - \frac{1}{100} \text{ mS}, \frac{11}{19} G_1 - \frac{1}{100} \text{ mS} \right]$$

$$G_2 G \left[\frac{3}{7} G_1 - \frac{1}{100} \text{ mS}, \frac{11}{19} G_1 - 1 \text{ mS} \right]$$

$$\frac{1}{R_2} G \left[\frac{3}{7} G_1 - \frac{1}{100} \text{ mS}, \frac{11}{19} G_1 - 1 \text{ mS} \right] \Rightarrow R_2 G \left[\frac{1}{\frac{11}{19} G_1 - 1 \text{ mS}} \cdot \frac{1}{\frac{3}{7} G_1 - \frac{1}{100} \text{ mS}} \right]$$

$$\text{i)} \left\{ \begin{array}{l} \frac{3}{7} G_1 - \frac{1}{100} \text{ mS} \geq 0 \Rightarrow G_1 \geq \frac{7}{300} \text{ mS} \\ \frac{3}{7} G_1 - \frac{1}{100} \text{ mS} \leq \frac{11}{19} G_1 - 1 \text{ mS} \Rightarrow \left(\frac{11}{19} - \frac{3}{7} \right) G_1 \geq \frac{99}{100} \text{ mS} \end{array} \right.$$

$$\Rightarrow G_1 \geq \frac{99}{100} \times \frac{133}{20} \Rightarrow G_1 \geq \frac{13167}{2000} \Rightarrow G_1 \geq 6.5835 \text{ mS}$$

$$R_1 \leq \frac{1}{G_1} \Rightarrow R_1 \leq 0.15189$$

$$\text{i)} R_1 (\text{mOhm}) = 0.15189 \text{ kOhm} \quad R_2 (\text{mOhm}) = \frac{1}{\frac{3}{7} G_1 + 109} - \frac{1}{100} \text{ mS} = 0.35567 \text{ kOhm}$$

$$P = IV = \frac{V^2}{R^2} \Rightarrow P = \frac{V^2}{R_1 + R_2} \text{ (min)} \Rightarrow R_1 + R_2 (\text{mOhm})$$

$$P (\text{mW}) = \frac{(6 \text{ V})^2}{0.15189 + 0.35567 \text{ kOhm}} = 70.928 \times 10^{-3} \text{ W}$$

$$R_{\text{eff}} = \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} = 0.10644 \text{ kOhm} \quad I_{\text{ao}} = 6 \text{ V} \cdot G_1 = 6 \text{ V} / R_1 = 39.502 \times 10^{-3} \text{ A}$$

$$P_N = I^2 \cdot R = I_{\text{ao}}^2 \cdot R_{\text{eff}} = 0.16609 \text{ W}$$

The power of original circuit and Norton circuit are not equal

10. Fandery Cheung 3033207855

Samuel Karmeschans 23804699

Cong Yang 3032217722

Untitled

July 16, 2017

In [6]: `import numpy as np`

In [11]: `a = np.array([[1, -1, 0, 0, -4000, 0, 0, 0, 0, 0],
[0, 1, -1, 0, 0, -3000, 0, 0, 0, 0],
[0, 1, 0, -1, 0, 0, -5000, 0, 0, 0],
[0, 0, 1, -1, 0, 0, 0, -2000, 0, 0],
[0, 0, 0, 1, 0, 0, 0, 0, -6000, 0],
[-1, 0, 0, 0, 0, 0, 0, 0, 0, 0],
[0, 0, 0, 0, -1, 1, 1, 0, 0, 0],
[0, 0, 0, 0, 0, -1, 0, 1, 0, 0],
[0, 0, 0, 0, 0, 0, -1, -1, 1, 0],
[0, 0, 0, 0, 0, 0, 0, 0, -1, 1]])`
`b = np.array([0, 0, 0, 0, -5, 0, 0.005, 0, -0.005])`

In [12]: `np.linalg.solve(a,b)`

Out[12]: `array([-5.00000000e+00, 1.46000000e+01, 2.12000000e+01,
1.56000000e+01, -2.40000000e-03, -2.20000000e-03,
-2.00000000e-04, 2.80000000e-03, 2.60000000e-03,
-2.40000000e-03])`

In []: